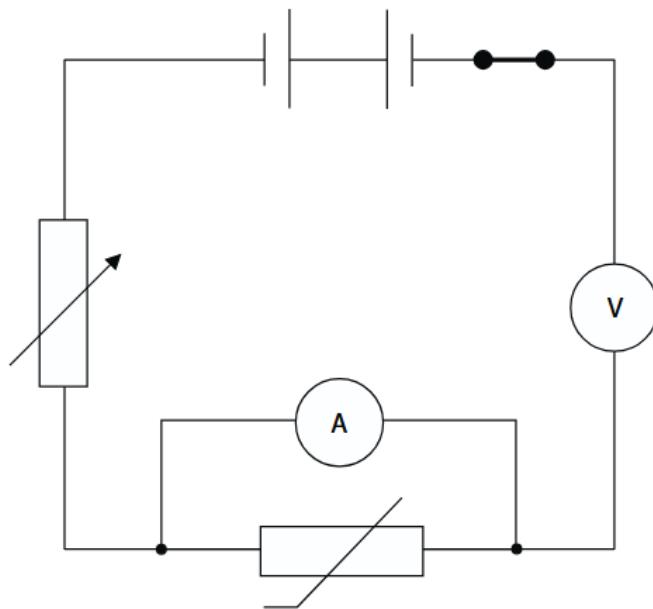


**3** A student investigates how the resistance of a thermistor varies with temperature.

(a) The student sets up the circuit shown in Figure 5 to measure current and voltage.

He finds that it does not work.



**Figure 5**

Give **three** modifications the student should make to the circuit so that the circuit works correctly.


(3)

1.....

2.....

3.....

- (b) The student uses the equipment shown in Figure 6 to measure the temperature of the thermistor.

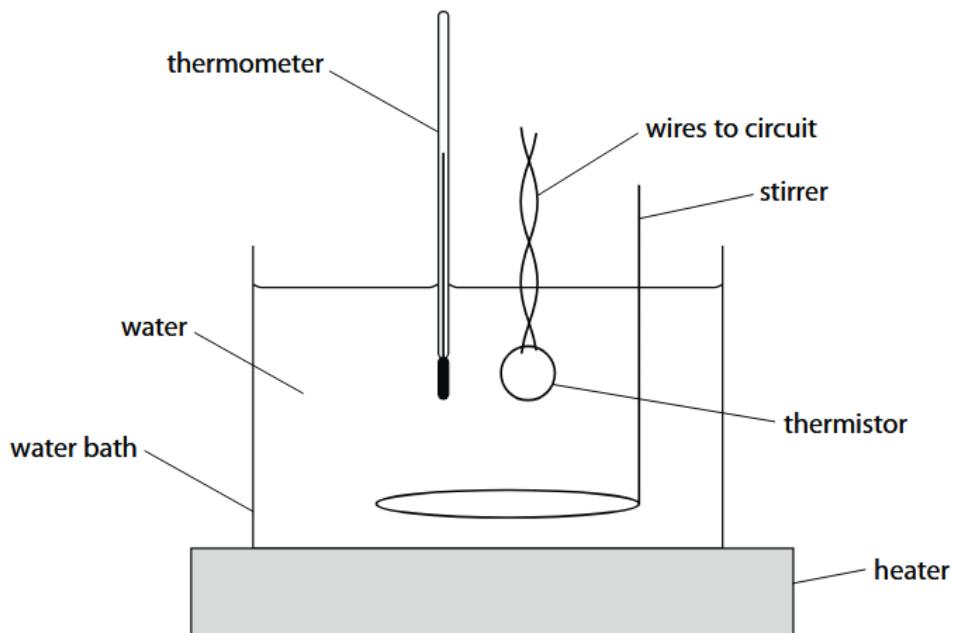

**Figure 6**

- (i) Give **one** reason for using the water bath.

(1)

---

---

- (ii) The equipment shown in Figure 6 is for investigations in the temperature range from 20°C to 100°C.

State **one** way the student could develop this experimental procedure to investigate temperatures outside this range.


(1)

---

---

(c) The student takes measurements for two other components, A and B.

The results for both these components are shown in Figure 7.

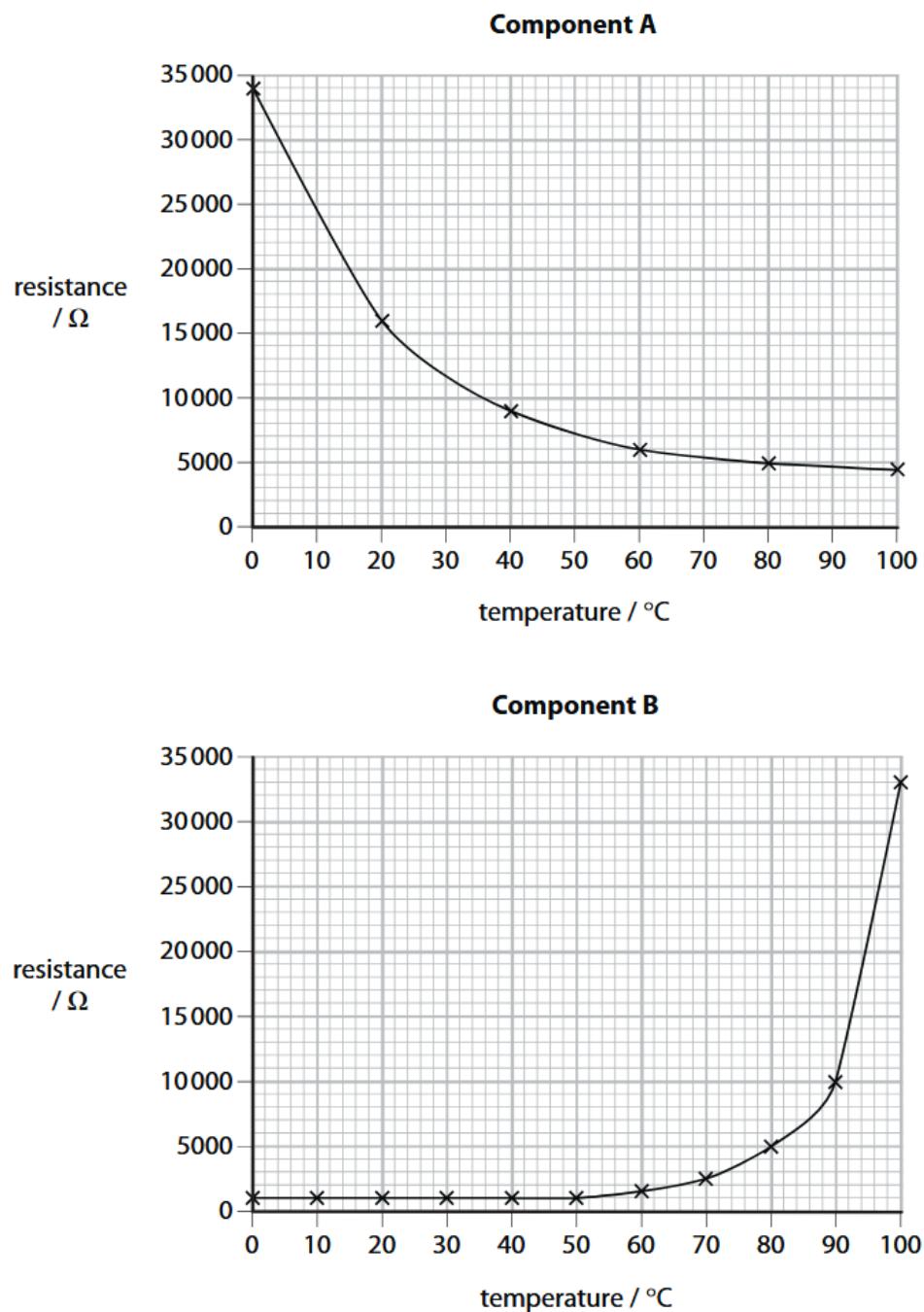

**Figure 7**

- (i) Compare and contrast how the resistances of component A and component B vary with temperature.

(3)

---

---

---

---

---

---

- (ii) Component A is connected to a 12V supply.

Which of these is the current in component A when the temperature is 80 °C?

(1)

A  $I = 12 \times 5000$

B  $I = \frac{12}{5000}$

C  $I = \frac{12^2}{5000}$

D  $I = \sqrt{\left(\frac{12}{5000}\right)}$

(Total for Question 3 = 9 marks)

---

<b>Question number</b>	<b>Answer</b>	<b>Additional guidance</b>	<b>Mark</b>
<b>3(a)</b>	<ul style="list-style-type: none"> <li>connect ammeter in series (with thermistor) (1)</li> <li>connect voltmeter in parallel (with thermistor) (1)</li> <li>reverse (connections for) one of the cells (1)</li> </ul>	allow idea that meters should be swapped for two marks (equivalent to first two points)	<b>(3)</b>

<b>Question number</b>	<b>Answer</b>	<b>Additional guidance</b>	<b>Mark</b>
<b>3(b)(i)</b>	<p>Any one of the following reasons:</p> <ul style="list-style-type: none"> <li>the thermistor and the water are at the same temperature (1)</li> <li>large volume of water gives a steady temperature rise (1)</li> </ul>	<p>accept idea that only small part of thermometer would be in contact with a thermistor in air</p> <p>accept difficult to control change in temperature of thermistor when heated in air</p>	<b>(1)</b>

<b>Question number</b>	<b>Answer</b>	<b>Additional guidance</b>	<b>Mark</b>
<b>3(b)(ii)</b>	<p>Any one of the following developments to the procedure:</p> <ul style="list-style-type: none"> <li>add ice to increase lower limit of temperature range (1)</li> <li>use liquid with higher boiling point to increase upper limit of temperature range (1)</li> </ul>	accept named liquid with higher boiling point, e.g. oil	<b>(1)</b>

<b>Question number</b>	<b>Answer</b>	<b>Additional guidance</b>	<b>Mark</b>
<b>3(c)(i)</b>	<p>A comparison and contrast that must include at least <b>one</b> similarity and <b>one</b> difference from the following points to a maximum of three marks:</p> <p>Similarities</p> <ul style="list-style-type: none"> <li>resistance of both changes with temperature (1)</li> <li>both graphs show a non-linear relationship (1)</li> <li>data comparison, e.g. both have the same resistance at 80°C (1)</li> </ul>		<b>(3)</b>

	<p>Differences</p> <ul style="list-style-type: none"> <li>• resistance of <b>A</b> decreases with temperature but resistance of <b>B</b> increases with temperature (1)</li> <li>• for <b>A</b>, (largest slope/rate of change) is at lower temperature but for <b>B</b>, (largest slope/rate of change) is at higher temperature(s) (1)</li> <li>• for <b>B</b>, resistance is constant below 50°C but for <b>A</b> resistance is roughly constant above 60°C (1)</li> </ul>	<p>accept (smallest slope/rate of change) for A is at higher temperature but (smallest slope/rate of change) for B is at lower temperature</p>	
--	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------	--

Question number	Answer	Mark
<b>3(c)(ii)</b>	B	<b>(1)</b>